

HW 4

Handong university

Jong-won Lee

- 1. For $f(A, B, C) = \prod M(0, 4, 6, 7)$
 - ▣ (a) Express it in algebraic expression of Product of maxterms.
 - ▣ (b) Draw a k-map.
 - ▣ (c) Express it in minimum POS expressions

- 2. Find minimum POS for each of the following equations.
 - (a) $f(a, b, c) = \prod M(1, 2, 3, 6)$
 - (b) $f(a, b, c, d) = \sum m(4, 6, 9, 10, 11, 12, 13) + \sum d(2, 15)$
 - (c) $f(a, b, c, d) = \prod M(1, 3, 5, 13) \cdot \prod D(0, 7, 9)$
 - (D) represents don't care conditions in maxterms.)

- 3. Ex. 1: Determine minimum SOP expression for the following Boolean expression using the Quine-McClusky algorithm. (15점)
(각 단계별 풀이 과정을 포함하여야 합니다.)

$$f(a, b, c, d) = \sum m(4, 5, 6, 8, 9, 10, 13) + \sum d(0, 7, 15)$$

- 4. Design a 4-bit adder ($a_3a_2a_1a_0 + b_3b_2b_1b_0$) using full adders. And verify your circuit using logisim-evolution simulator.
 - ▣ (a) 디자인한 회로를 캡처하여 제출하여라. (10점)
 - ▣ (b) test vector를 이용하여 모든 입력에 대해서 회로가 정상적으로 동작함을 보이는 test 결과를 캡처하여 제출하여라. (10점)