

HW5

COMBINATIONAL SYSTEM 1


Handong university

Jong-won Lee

HW5

2

- 1. We are going to design a circuit to compute an odd parity of an n -bit binary number.
 - ▣ The odd parity is generated so that the number of 1's in the $(n+1)$ -bit binary number which is including the parity bit is odd.
 - ▣ (a) design a circuit to compute an odd parity of one-bit binary number.
 - Use only NAND gates and NOT gates.
 - Complemented input signals can not be used.
 - Input signals: a_i and p_i
 - Output signal: p_{i+1}

 

HW5


3

- 1. We are going to design a circuit to compute an odd parity of an n-bit binary number.
 - ▣ (b) design a circuit to compute an odd parity of a 3-bit binary number, (use the circuit designed in (a)) and verify it's operation by logisim-evolution.
 - ▣ (c) Determine the delay to compute an odd parity of an n-bit binary number.

HW5

4

 - 2. (a) Design active high 3-to-8 decoder using active high 2-to-4 decoder with enable.
 - Use minimum number of IC's.
 - Can use general gates such as NOT, NAND, and NOR when they are absolutely necessary.
 - Inputs: abc (a: MSB)



EN'	a	b	Y ₀	Y ₁	Y ₂	Y ₃
1	x	x	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1

HW5

5

- 2. (b) Design a circuit for f and g using active high 3-to-8 decoder designed in the problem 2(a).
 - ▣ $f(a,b,c)=\sum m(1, 3, 6), \quad g(a,b,c)=\sum m(0,4,7)$

HW5

6

- 3. Design a 4-to-2 priority encoder with the following truth table.

A3	A2	A1	A0	z1	z0
0	x	x	x	1	1
1	0	x	x	1	0
1	1	0	x	0	1
1	1	1	0	0	0